

# Assignment No 8: Circuit Analysis using Sympy

Sharanesh R (EE19B116)

April 23, 2021

## Abstract

In this assignment we are supposed to:

- To analyze the Filters using Laplace Transform.
- Try out the various possible simulations using Sympy.
- To plot graphs to understand high pass and low pass analog filters.

## 1 Low Pass Filter

In this section, we analyze the following low pass filter circuit:

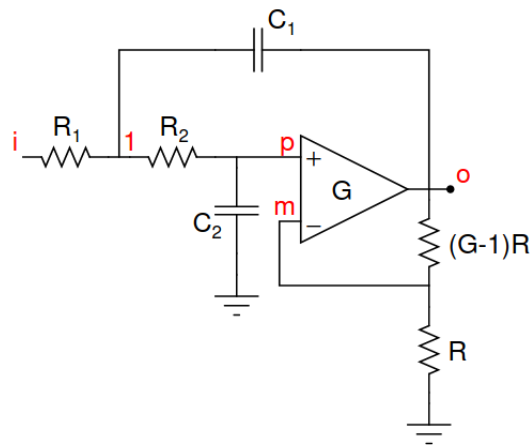


Figure 1: Op-Amp based Low-Pass Filter

When we apply KCL to the above circuit we get the following matrix equation,

$$\begin{pmatrix} 0 & 0 & 1 & -\frac{1}{G} \\ -\frac{1}{1+sR_2C_2} & 1 & 0 & 0 \\ 0 & -G & G & 1 \\ -\frac{1}{R_1} - \frac{1}{R_2} - sC_1 & \frac{1}{R_2} & 0 & sC_1 \end{pmatrix} \begin{pmatrix} V_1 \\ V_p \\ V_m \\ V_o \end{pmatrix} = \begin{pmatrix} 0 \\ 0 \\ 0 \\ -V_i(s)/R_1 \end{pmatrix}$$

We now solve the above matrix equation using `sympy` and the output **Vo** as an `sympy` expression, further we convert this `sympy` expression to a LTI system by decomposing it into fraction and recreating a LTI system.

The plot for the magnitude of the transfer function is as shown below,

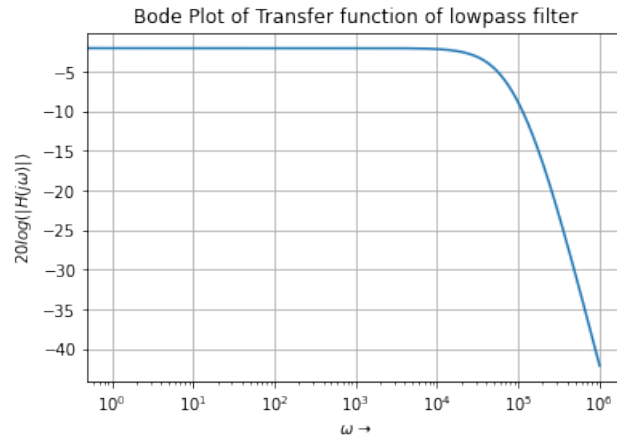


Figure 2: Magnitude bode plot of the low pass filter

To get the step response of the system, we use `signal.step`, and the plot of the same is shown below,

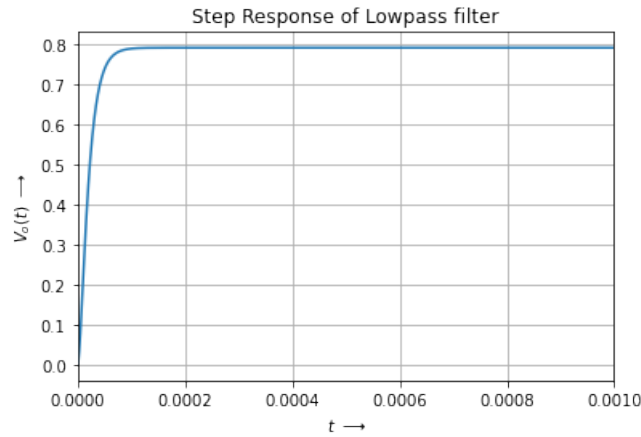


Figure 3: Step response of the low pass filter

For the given input  $V_i(t) = (\sin(2\pi \times 10^3 t) + \cos(2\pi \times 10^6 t))u(t)$ , the plot of the input and output of the low pass filter is,

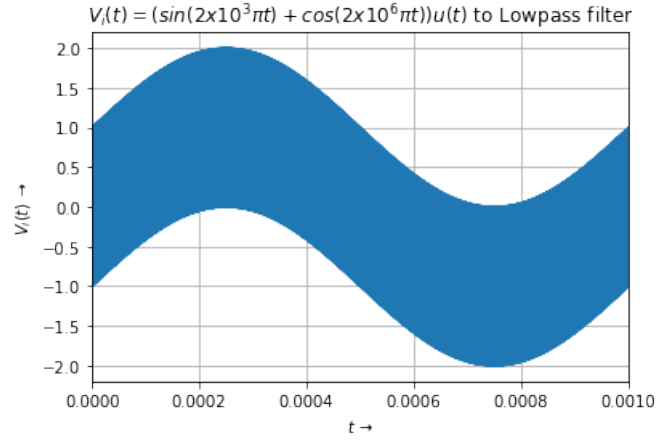


Figure 4: Input  $V_i(t)$  to the low pass filter

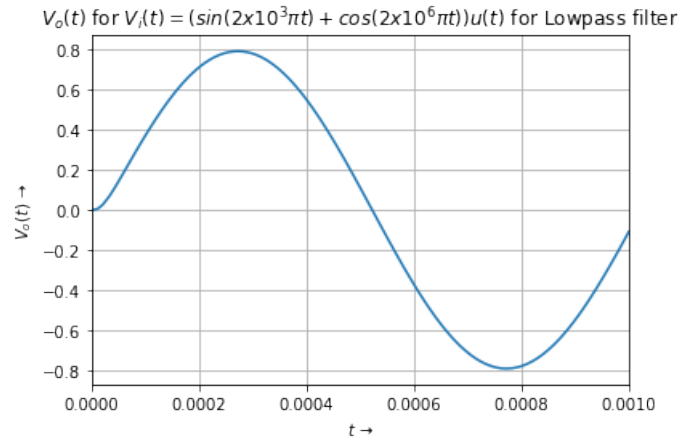


Figure 5: Output of the low pass filter for the given input  $V_i(t)$

## 2 High Pass Filter

In this section, we analyze the following low pass filter circuit:

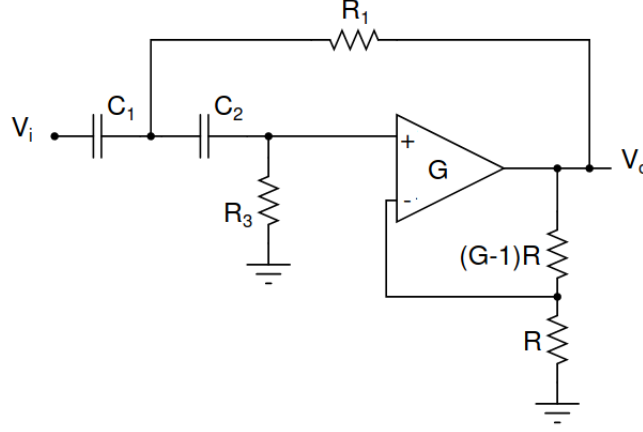


Figure 6: Op-Amp based High-Pass Filter

When we apply KCL to the above circuit we get the following matrix equation,

$$\begin{pmatrix} 0 & 0 & 1 & -\frac{1}{G} \\ -\frac{sR_3C_2}{1+sR_3C_2} & 1 & 0 & 0 \\ 0 & -G & G & 1 \\ -1 - (sR_1C_1) - (sR_3C_2) & sC_2R_1 & 0 & 1 \end{pmatrix} \begin{pmatrix} V_1 \\ V_p \\ V_m \\ V_o \end{pmatrix} = \begin{pmatrix} 0 \\ 0 \\ 0 \\ -V_i(s)sR_1C_1 \end{pmatrix}$$

We now solve the above matrix equation using **sympy** and the output **V<sub>o</sub>** as an sympy expression, further we convert this sympy expression to a LTI system by decomposing it into fraction and recreating a LTI system.

The plot for the magnitude of the transfer function is as shown below,

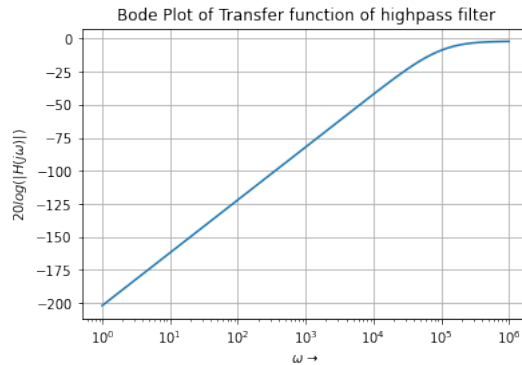


Figure 7: Magnitude bode plot of the high pass filter

To get the step response of the system, we use `signal.step`, and the plot of the same is shown below,

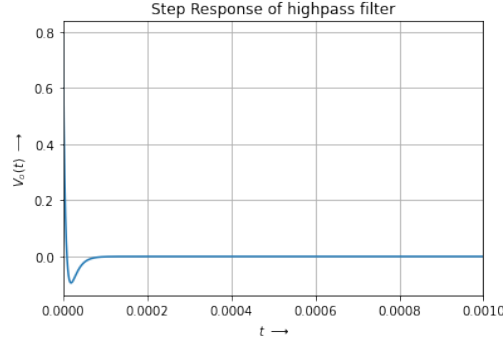


Figure 8: Step response of the high pass filter

For the given input  $V_i(t) = (\sin(2\pi \times 10^3 t) + \cos(2\pi \times 10^6 t))u(t)$ , the plot of the input and output of the high pass filter is,

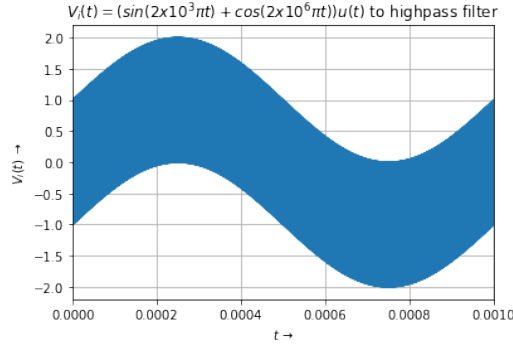


Figure 9: Input  $V_i(t)$  to the high pass filter

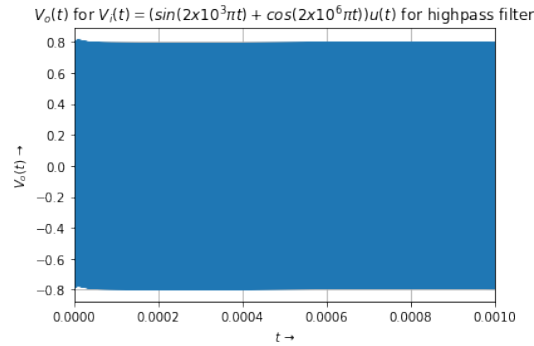


Figure 10: Output of the high pass filter for the given input  $V_i(t)$

## Damped Sinusoidal response

Here we try to observe the output of the High pass filter to the damped sinusoidal input. For this purpose, we consider two inputs damped sinusoids of frequencies 1 kHz and 1 MHz,

the low frequency input is:  $V_i(t) = e^{-10t}(\cos(200\pi t))u_o(t)$  Volts

the high frequency input is:  $V_i(t) = e^{-10t}(\cos(2000000\pi t))u_o(t)$  Volts

Now the response of the high pass filter to the above damped sinusoids alongwith the corresponding inputs is shown below,

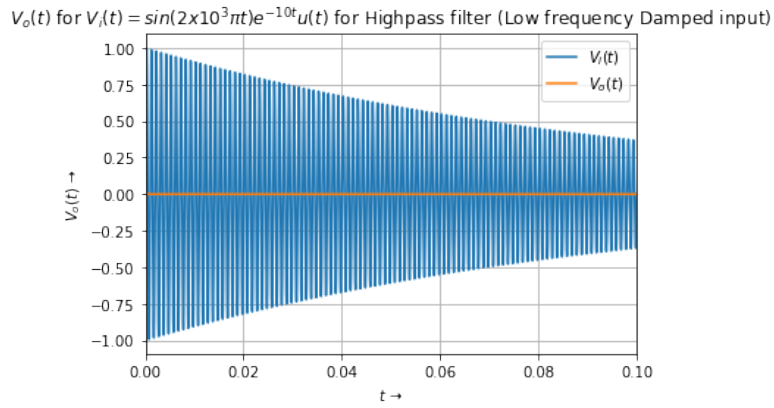


Figure 11: Low frequency damped response the high pass filter

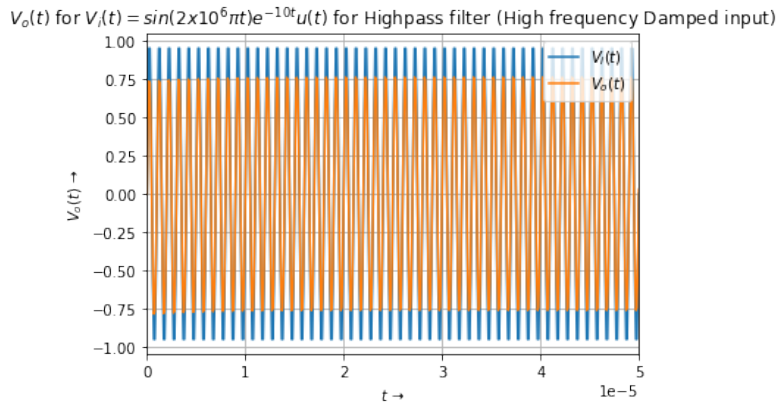


Figure 12: High frequency damped response the high pass filter

## Conclusion

In order to conclude, we have seen the following in this assignment,

1. Sympy provides a useful way to analyse LTI systems using the Laplace transforms.
2. We studied the behaviour of a low pass filter, realized using an operational amplifier model of same with gain  $G$ .
3. For a mixed frequency sinusoid as input, it was found that the filter suppressed the high frequencies while allowing the low frequency components.
4. Similarly, a high pass filter was implemented using an operational amplifier with the same gain  $G$ . The magnitude response of the filter was plotted and its output was analysed for damped sinusoids.
5. The step response of the filter was found to have a non-zero peak at  $t = 0$ , due to the sudden change in the input voltage (initial transients).
6. We have also visualized the response of the high pass filter to the given high and low frequency sinusoids. In this the output for the low frequency case was almost zero, while the output of the high frequency was attenuated.